


Instruction:

Complete all questions in **1 hour**.

1. Draw the logic diagram of the following gates using logsim and complete the Truth tables.

a) AND


| A | B | A.B |
|---|---|-----|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

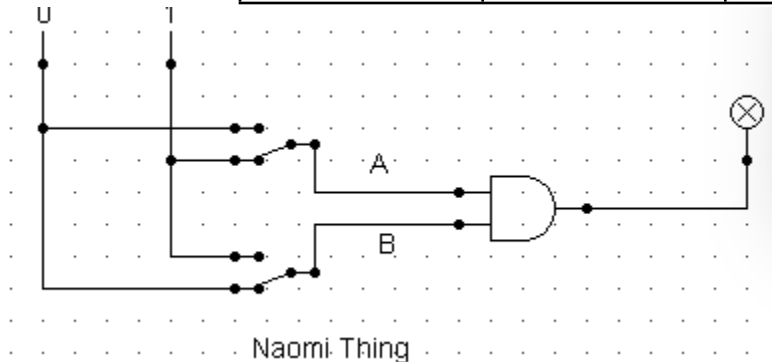

[Insert your gif image here]


b) NOR (do the same as in Q No a for all of the following)

| A | B | $(A+B)'$ |
|---|---|----------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

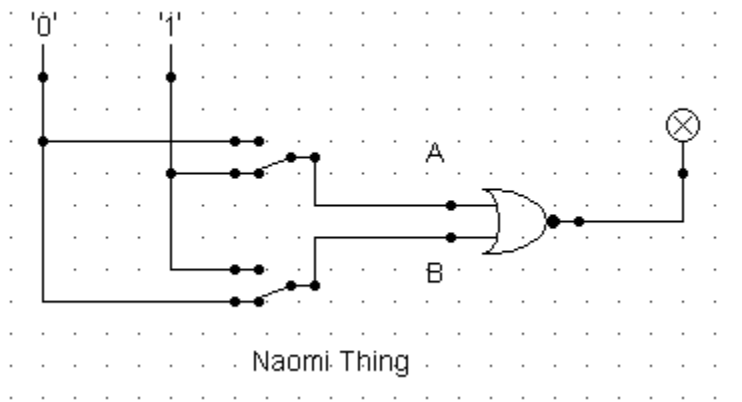

c) OR


| A | B | A+B |
|---|---|-----|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

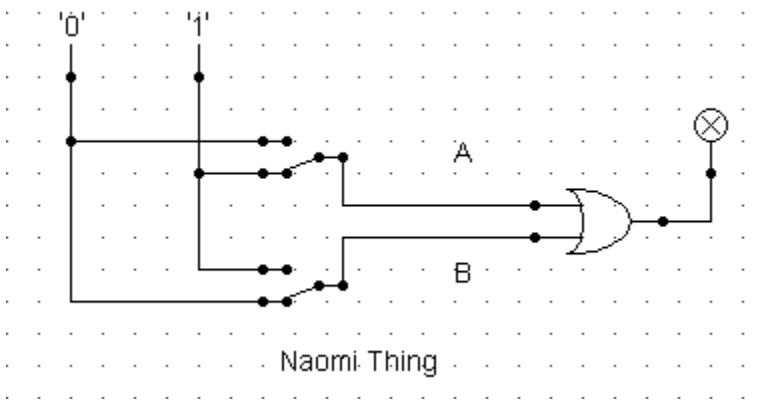

d) NAND (using NOT and AND)


| A | B | (A.B)' |
|---|---|--------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |

| | | |
|---|---|---|
| 1 | 1 | 0 |
|---|---|---|

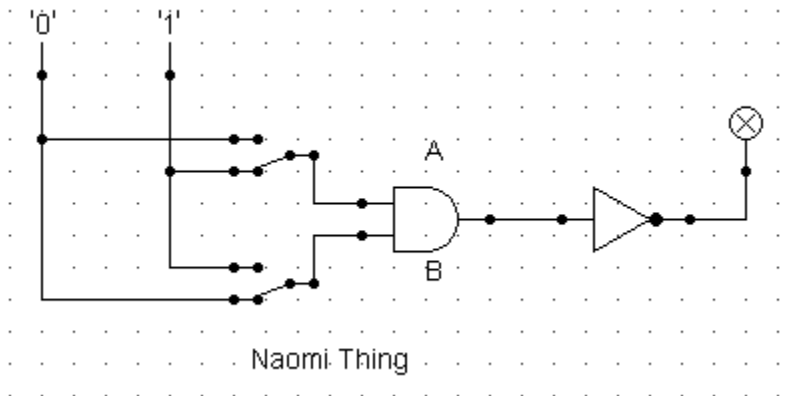

e) XOR using AOI

| A | B | $A'B + AB'$ |
|---|---|-------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

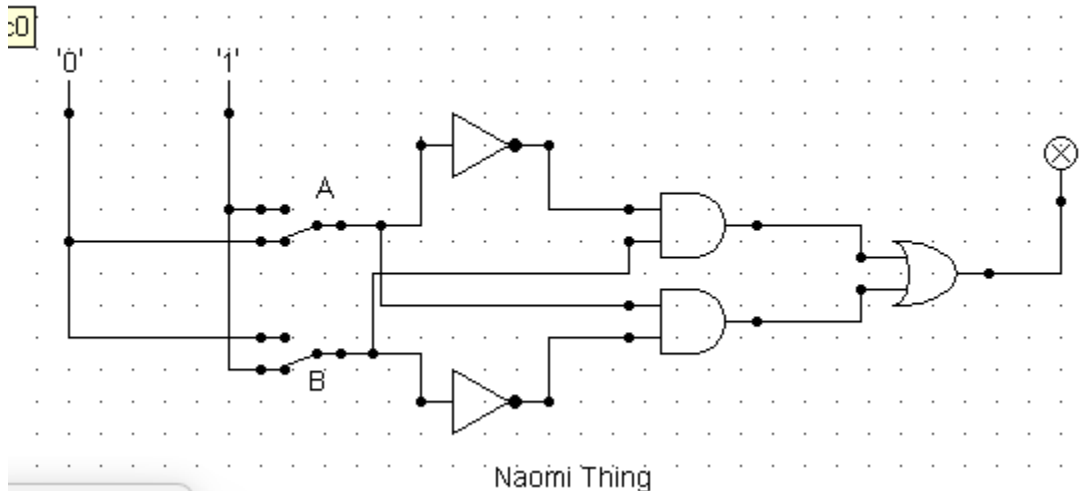


- Use LogSim to build the equivalent circuit for the following Boolean equations. Prove that the expressions are equivalent by computing truth table.



$$\neg(A + B) = \neg A \cdot \neg B$$

| A | B | $\neg(A+B)$ | $\neg A \cdot \neg B$ |
|---|---|-------------|-----------------------|
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 |


[Insert your gif image here]

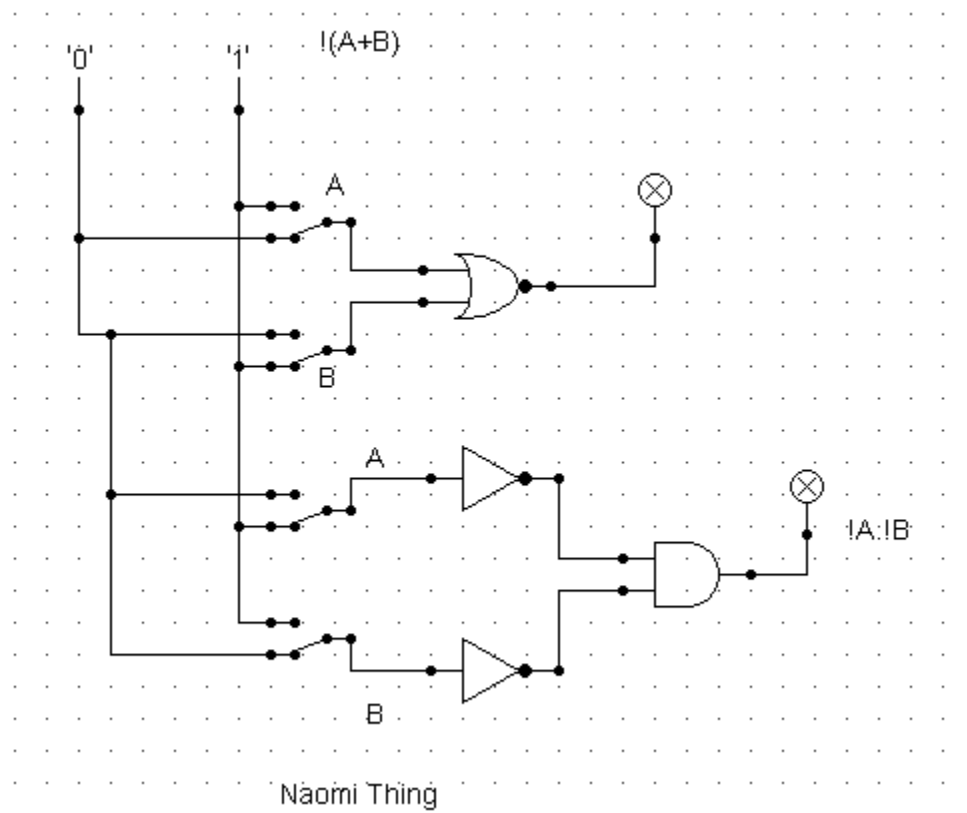

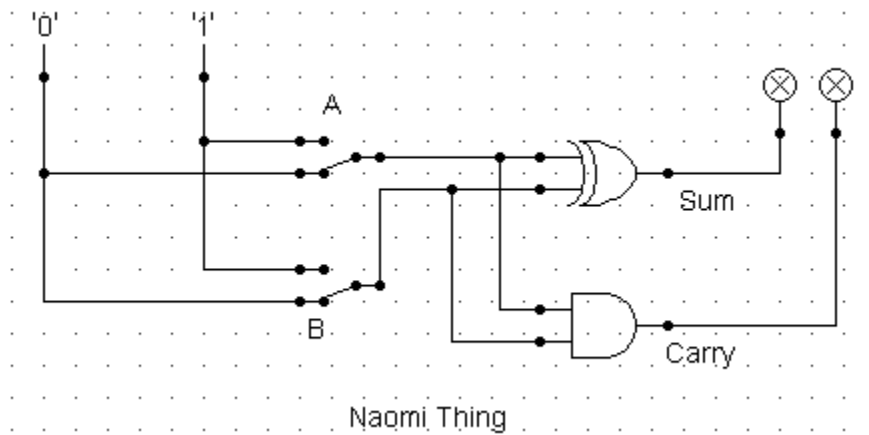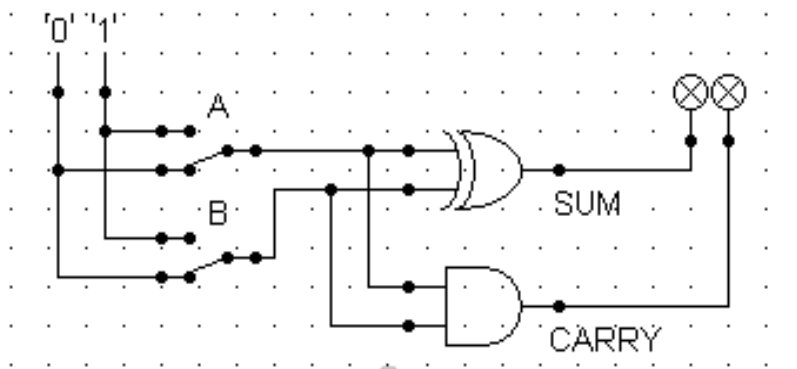3. Draw the following circuit of half adder using LogSim.



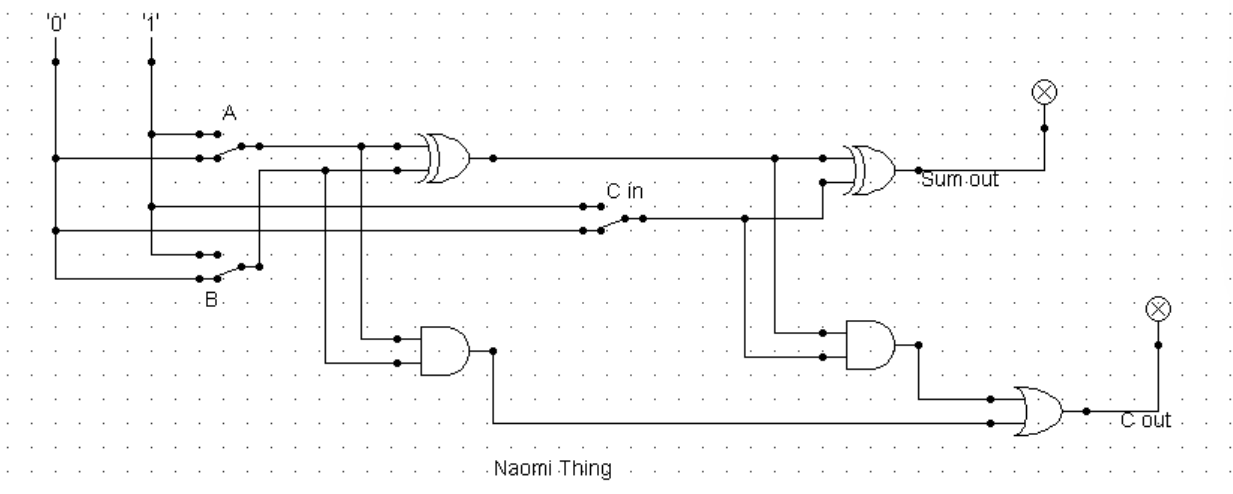
4. Draw full adder using Logsim and construct truth table.




| A | B | C | Sum | Carry |
|---|---|---|-----|-------|
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 |

5. Draw the logic circuit for the following Boolean equations using logsim simulator.

a. $AB+C$

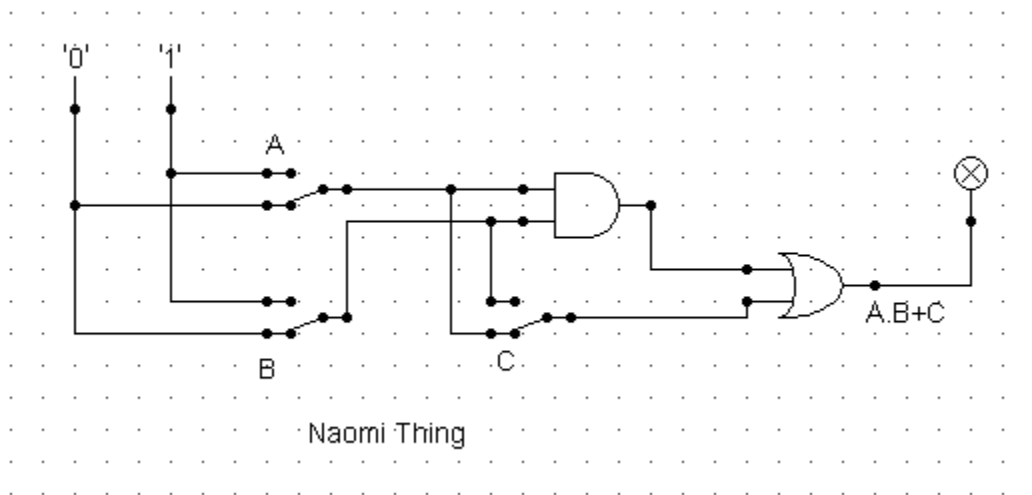

b. $A(B+C)$

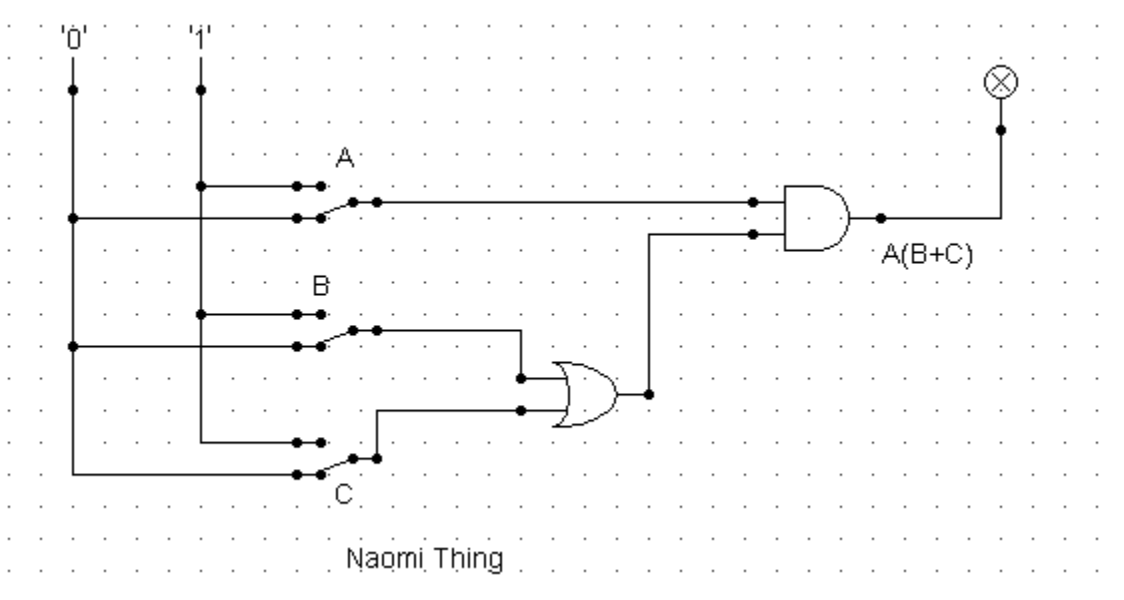

c. $X'Y'Z'$ 