


1.

- a. Define half adder.
  - The circuit that generates to carry and sum with two given inputs is known as half adder.
- b. Draw a truth table for the sum and carry of half adder.

A	B	Sum(S)	Carry(C)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- c. Write the sop expression from the truth table.
  - The SOP for sum is  $A \oplus B$  and for Carry is  $A.B$
- d. Draw the circuit using logsim.

*[Paste your gif image here]*

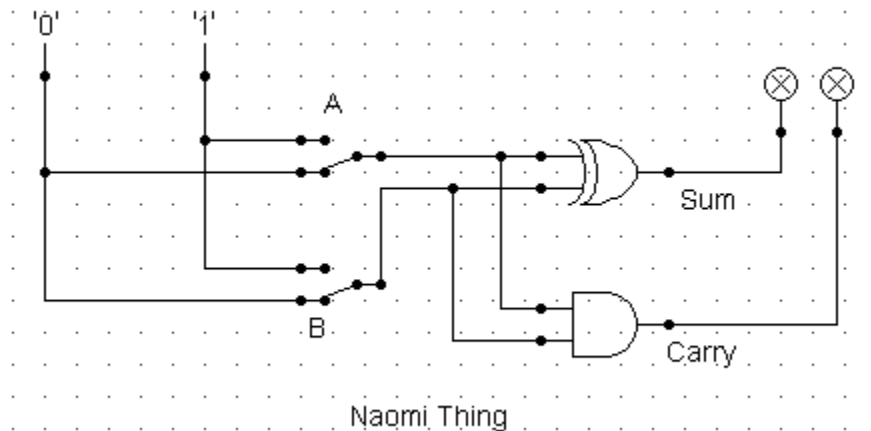

2.

- a. Draw the truth table for the outputs of the full adder.

A	B	C(in)	Sum(S)	Carry[C(out)]
0	0	0	0	0

1	0	0	1	0
0	1	0	1	0
1	1	0	0	1
0	0	1	1	0
1	0	1	0	1
0	1	1	0	1
1	1	1	1	1

- b. Write the corresponding sop expression for sum and carry of full adder and simplify the expression

-SOP expression of Sum =  $A'B'C + AB'C' + A'BC' + ABC$

=  $A'(B'C + BC') + A(B'C' + BC)$

=  $A'(B \oplus C) + A(B \oplus C)'$

let  $B \oplus C = X$

so;

=  $A'X + AX'$

=  $A \oplus X$

=  $A \oplus B \oplus C$

- SOP expression of Carry =  $A'BC + AB'C' + ABC$


=  $A'BC + ABC + AB'C' + ABC + ABC' + ABC$

=  $BC(A' + A) + AC(B' + B) + AB(C' + C)$

=  $AB + BC + AC$

- c. Draw full adder using two half adder and an OR gate.

*[Paste your gif image here]*

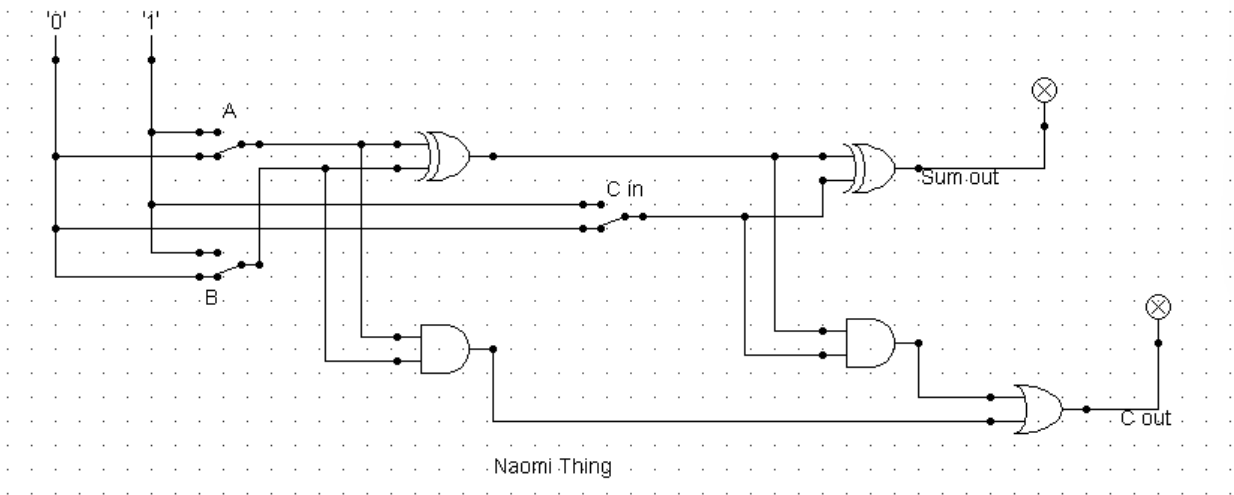


3. Using the three stages of design, construct the circuits for the following input /output values. Here A, B and C are the inputs whereas D, E, F, G, H and I are outputs. *Note: Draw circuit diagram using logsim corresponding to the simplified expression of outputs D, E, F, G, H and I.*

A	B	C	D	E	F	G	H	I
0	0	0	1	0	1	0	1	1
0	0	1	1	0	1	1	0	1
0	1	0	1	0	1	1	1	1
1	0	0	1	0	0	1	0	1
1	1	1	1	1	1	1	1	1
1	1	0	1	1	0	1	0	1
1	0	1	1	1	1	1	1	0
0	1	1	0	0	0	1	1	1

*[Paste your gif images here]*

ans:


POS of  $D = A + B' + C'$

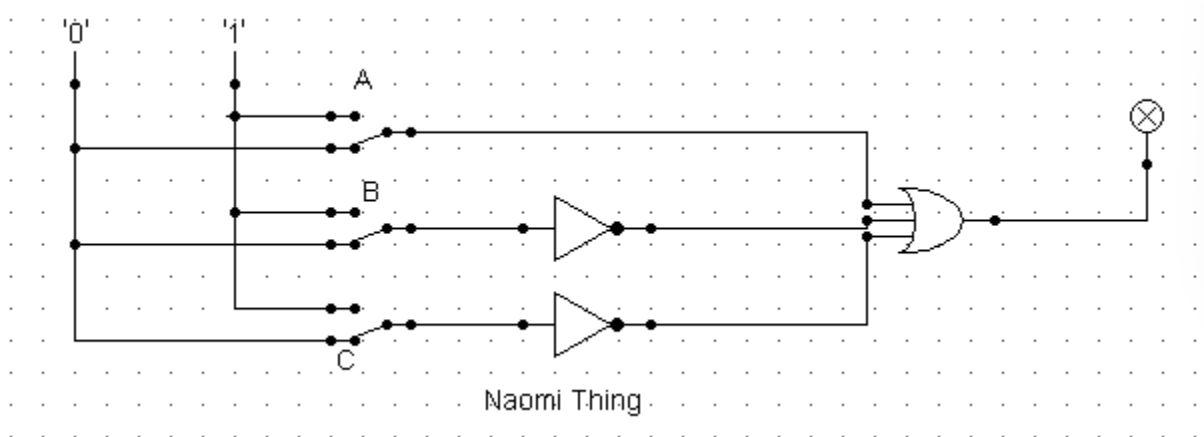

SOP of  $E = ABC + ABC' + AB'C$

$$= AB(C + C') + AB'C$$


$$= AB + AB'C$$

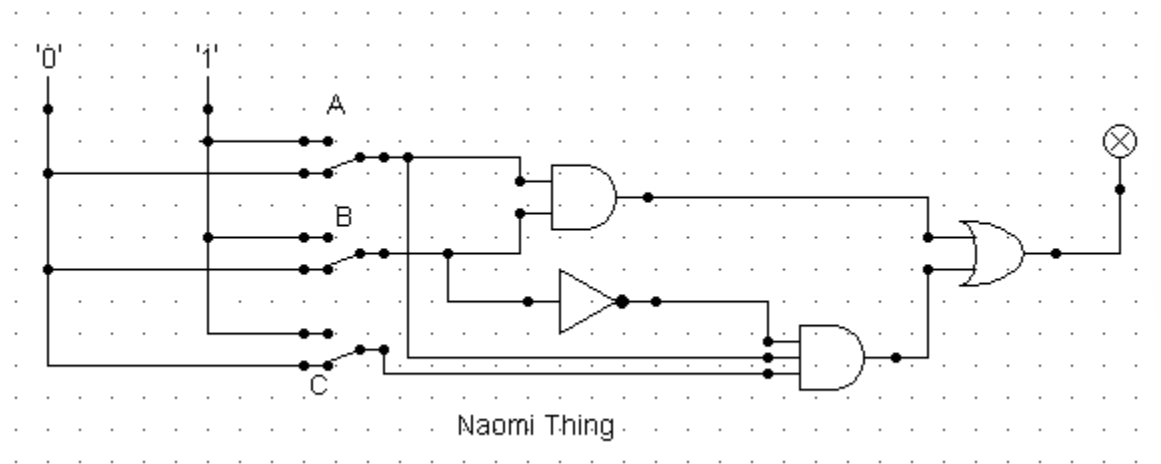


SOP of  $F = A'B'C' + A'B'C + A'BC' + ABC + AB'C$

$$= A'B'(C' + C) + A'BC' + AC(B + B')$$

$$= A'B' + A'BC' + AC$$

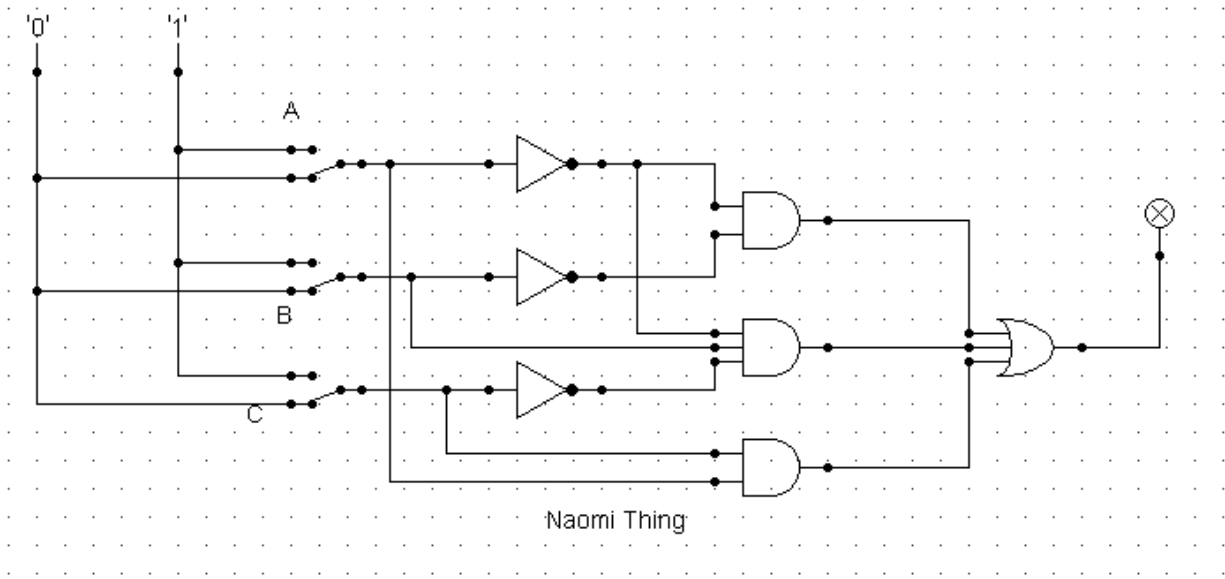


POS of  $G = A + B + C$

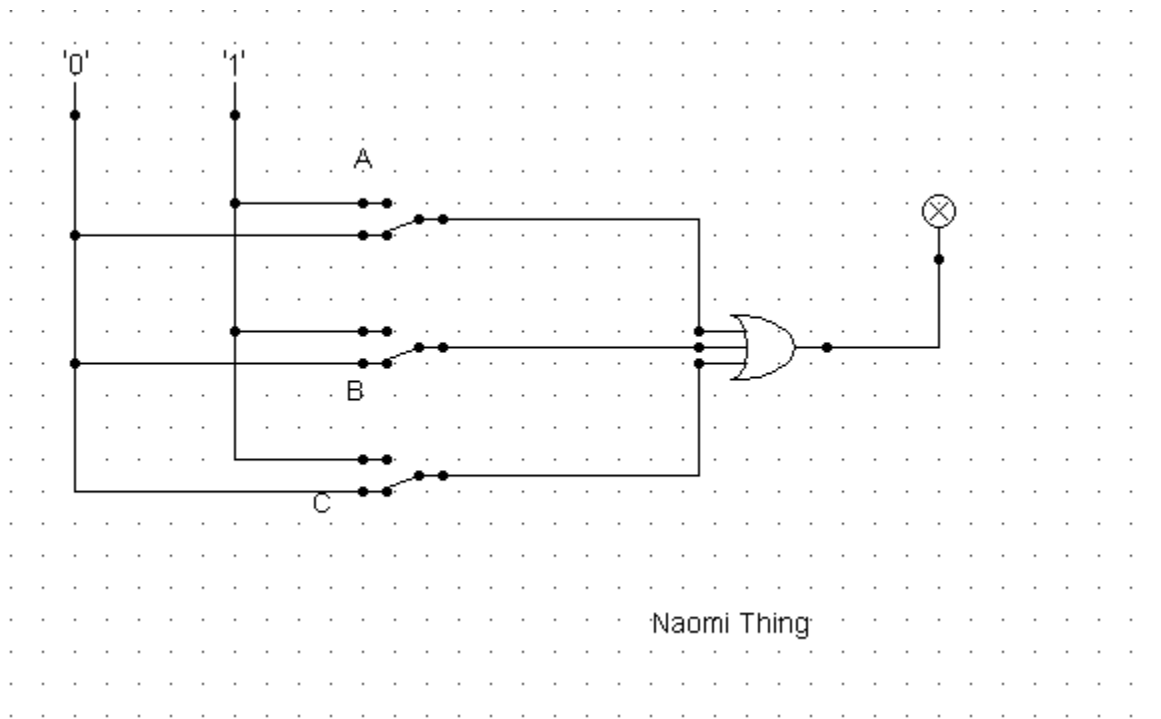

SOP of  $H = A'B'C' + A'BC' + ABC + AB'C + A'BC$

$$= A'C'(B' + B) + BC(A + A') + AB'C$$

$$= A'C' + BC + AB'C$$

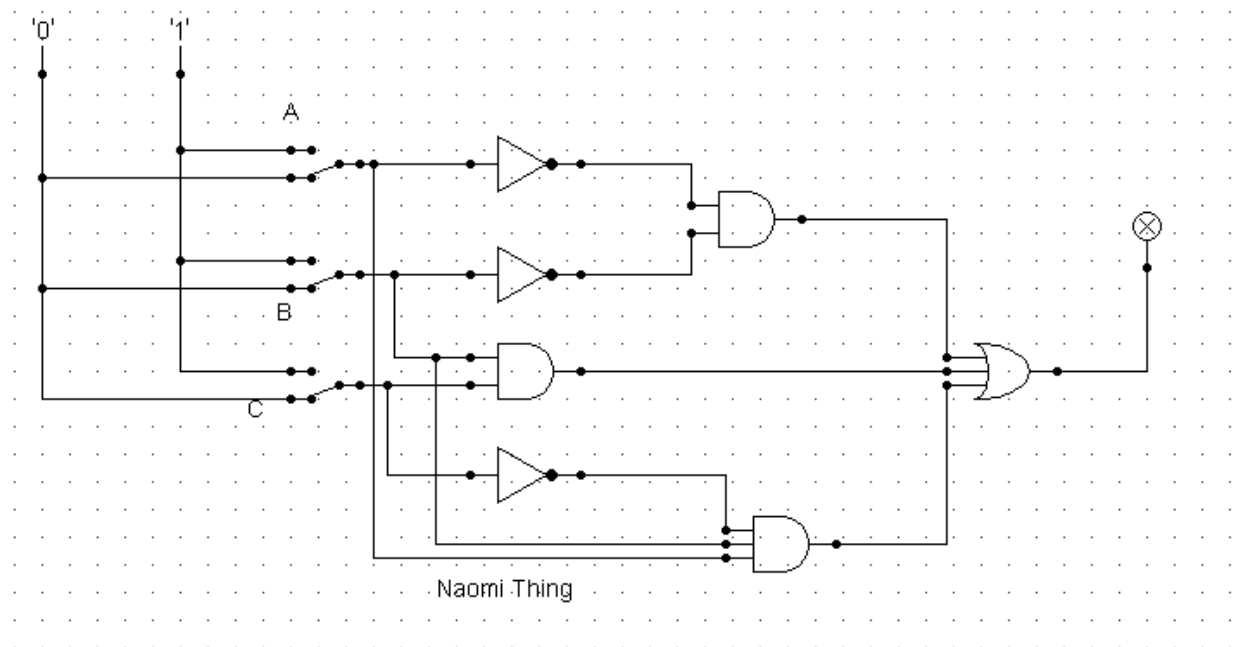

POS of  $I = A' + B + C'$

